

| LESSON PLAN (WINTER-2023) | | | |
|---|----------|-------------------------------|--|
| Discipline: Electrical | | Semester:5 th Sem | Name of the Teaching Faculty: Mrs. Jayashree Mohanty (Sr. Lect. Electrical Engg) |
| Subject: Power Electronics and PLC | Date | Theory Periods: 4P/Week | Semester From Date:-01.08.23 to Date:- 30.11.23 No. of Weeks:18 |
| 1st Week | 02.08.23 | 1st | Construction, Operation, V-I characteristics & application of power diode |
| | 04.08.23 | 2nd | Construction, Operation, V-I characteristics & application of SCR |
| | 05.08.23 | 3rd | Construction, Operation, V-I characteristics & application of DIAC |
| 2nd Week | 07.08.23 | 1st | Construction, Operation, V-I characteristics & application of TRIAC |
| | 09.08.23 | 2nd | Construction, Operation, V-I characteristics & application of Power MOSFET |
| | 11.08.23 | 3rd | Construction, Operation, V-I characteristics & application of GTO |
| | 12.08.23 | 4th | Construction, Operation, V-I characteristics & application of IGBT |
| 3rd Week | 14.08.23 | 1st | Two transistor analogy of SCR, Gate characteristics of SCR. |
| | 16.08.23 | 2nd | Switching characteristic of SCR during turn on and turn off. |
| | 18.08.23 | 3rd | Turn on methods of SCR |
| | 19.08.23 | 4th | Turn off methods of SCR (Line commutation and Forced commutation) (i) Load Commutation (ii) Resonant pulse commutation |
| 4th Week | 21.08.23 | 1st | Voltage and Current ratings of SCR, Protection of SCR, Over voltage protection |
| | 23.08.23 | 2nd | Over current protection, Gate protection |
| | 25.08.23 | 3rd | Firing Circuits, General layout diagram of firing circuit |
| | 26.08.23 | 4th | R firing circuits |
| 5th Week | 28.08.23 | 1st | R-C firing circuit |
| | 01.09.23 | 2nd | UJT pulse trigger circuit, Synchronous triggering (Ramp Triggering) |
| | 02.09.23 | 3rd | Design of Snubber Circuits |
| 6th Week | 04.09.23 | 1st | Controlled rectifiers Techniques (Phase Angle, Extinction Angle control), Single |
| | 08.09.23 | 2nd | Working of single-phase half wave controlled converter with R-L loads, Understand need of freewheeling diode. |
| | 09.09.23 | 3rd | Working of single phase fully controlled converter with resistive and R- L loads. |
| 7th Week | 11.09.23 | 1st | Working of single phase fully controlled converter with resistive and R- L loads. |
| | 13.09.23 | 2nd | Working of three-phase half wave controlled converter with Resistive load |
| | 15.09.23 | 3rd | Working of three phase fully controlled converter with resistive load |
| | 16.09.23 | 4th | Working of single phase AC regulator |
| 8th Week | 18.09.23 | 1st | Working principle of step up & step down chopper |
| | 22.09.23 | 2nd | Control modes of chopper, Operation of chopper in all four quadrants. |
| | 23.09.23 | 3rd | Operation of chopper in all four quadrants. |
| 9th Week | 25.09.23 | 1st | Operation of chopper in all four quadrants. |
| | 27.09.23 | 2nd | Operation of chopper in all four quadrants. |
| | 30.09.23 | 3rd | Classify inverters, Explain the working of series inverter. |
| 10th Week | 04.10.23 | 1st | Explain the working of parallel inverter |
| | 06.10.23 | 2nd | Explain the working of single-phase bridge inverter. |
| | 07.10.23 | 3rd | Explain the basic principle of Cyclo-converter, Explain the working of single-phase step up & step down Cyclo-converter, Applications of Cyclo-converter |

| | | | |
|-----------|----------|-----|--|
| 11th Week | 09.10.23 | 1st | List applications of power electronic circuits, List the factors affecting the speed of DC Motors, Speed control for DC Shunt motor using converter. |
| | 11.10.23 | 2nd | Speed control for DC Shunt motor using chopper |
| | 13.10.23 | 3rd | List the factors affecting speed of the AC Motors, Speed control of Induction Motor by |
| | 14.10.23 | 4th | Speed control of induction motor by using converters and inverters (V/F control). |
| 12th Week | 16.10.23 | 1st | Working of UPS with block diagram. |
| | 18.10.23 | 2nd | Battery charger circuit using SCR with the help of a diagram |
| | 20.10.23 | 3rd | Basic Switched mode power supply (SMPS) - explain its working & applications |
| 14th Week | 30.10.23 | 1st | Introduction of Programmable Logic Controller (PLC), Advantages of PLC, Different parts of |
| | 01.11.23 | 2nd | Assignment |
| | 03.11.23 | 3rd | Ladder diagram, Description of contacts and coils in the following states |
| | 04.11.23 | 4th | Ladder diagrams for combination circuits using NAND, NOR, AND, OR and NOT |
| 15th Week | 06.11.23 | 1st | Timers-i) T ON ii) T OFF and iii) Retentive timer |
| | 08.11.23 | 2nd | Counters-CTU, CTD, Ladder diagrams using Timers and counters |
| | 10.11.23 | 3rd | PLC Instruction set, Ladder diagrams for following |
| | 11.11.23 | 4th | (ii) Stair case lighting |
| 16th Week | 13.11.23 | 1st | (iii) Traffic light Control |
| | 15.11.23 | 2nd | (iv) Temperature Controller |
| | 17.11.23 | 3rd | Special control systems- Basics DCS |
| | 18.11.23 | 4th | SCADA systems |
| 17th Week | 20.11.23 | 1st | Computer Control-Data Acquisition |
| | 22.11.23 | 2nd | Direct Digital Control System (Basics only) |
| | 24.11.23 | 3rd | Tutorial |
| | 25.11.23 | 4th | Tutorial |
| 18th Week | 29.11.23 | 1st | Tutorial |

Anshu
 31.07.2023
 (Sr. Lect. - Elect)