

UNIT 4

BIASING AND STABILIZATION

TRANSISTOR BIASING:

To operate the transistor in the desired region, we have to apply external DC voltages of correct polarity and magnitude to the two junctions of the transistor. This is known as biasing of the transistor.

Since DC voltages are used to bias the transistor, it is called as DC biasing.

DC OPERATING POINT (OR) QUIESCENT POINT:

Application of DC voltages (bias) establishes a fixed level of current and voltage. For transistor amplifiers the resulting DC current and voltage establish an **operating point** on the characteristics that define the region that will be employed for amplification of the applied signal. Since the operating point is a fixed point on the characteristics, it is called as Quiescent point (Q - Point).

Note: Quiescent → Still inactive and quiet.

NEED FOR BIASING:


- To operate the transistor in the desired region.
- The DC sources supply the power to the transistor circuit, to get the output signal power greater than the input signal power.

LOAD LINE:

- It is a straight line drawn on the characteristic curve with two end points A and B.
- It is used to fix the operating point of a transistor.



TYPES OF LOAD LINE:

- DC load line
- AC load line

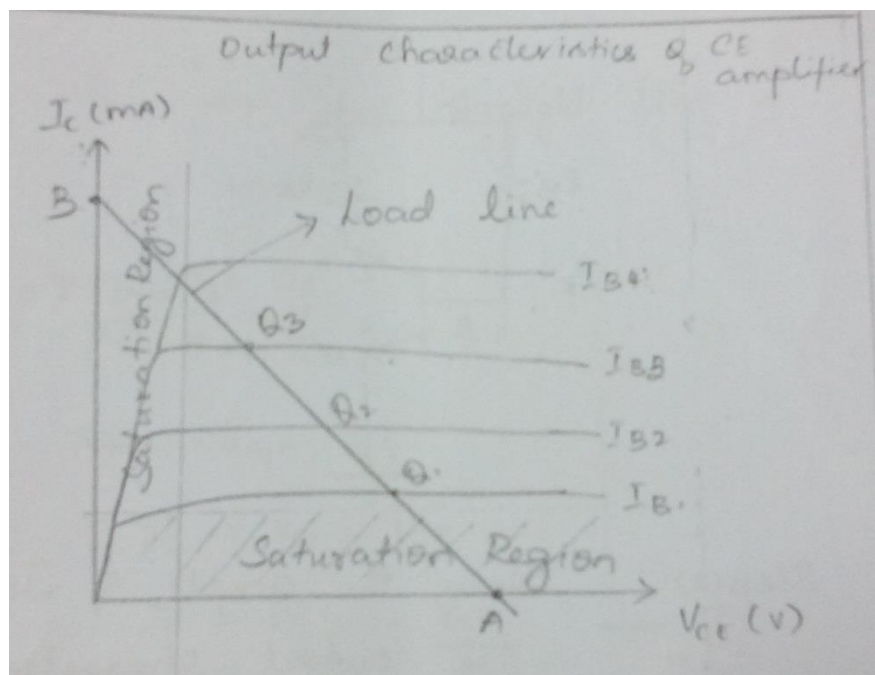

DC LOAD LINE:

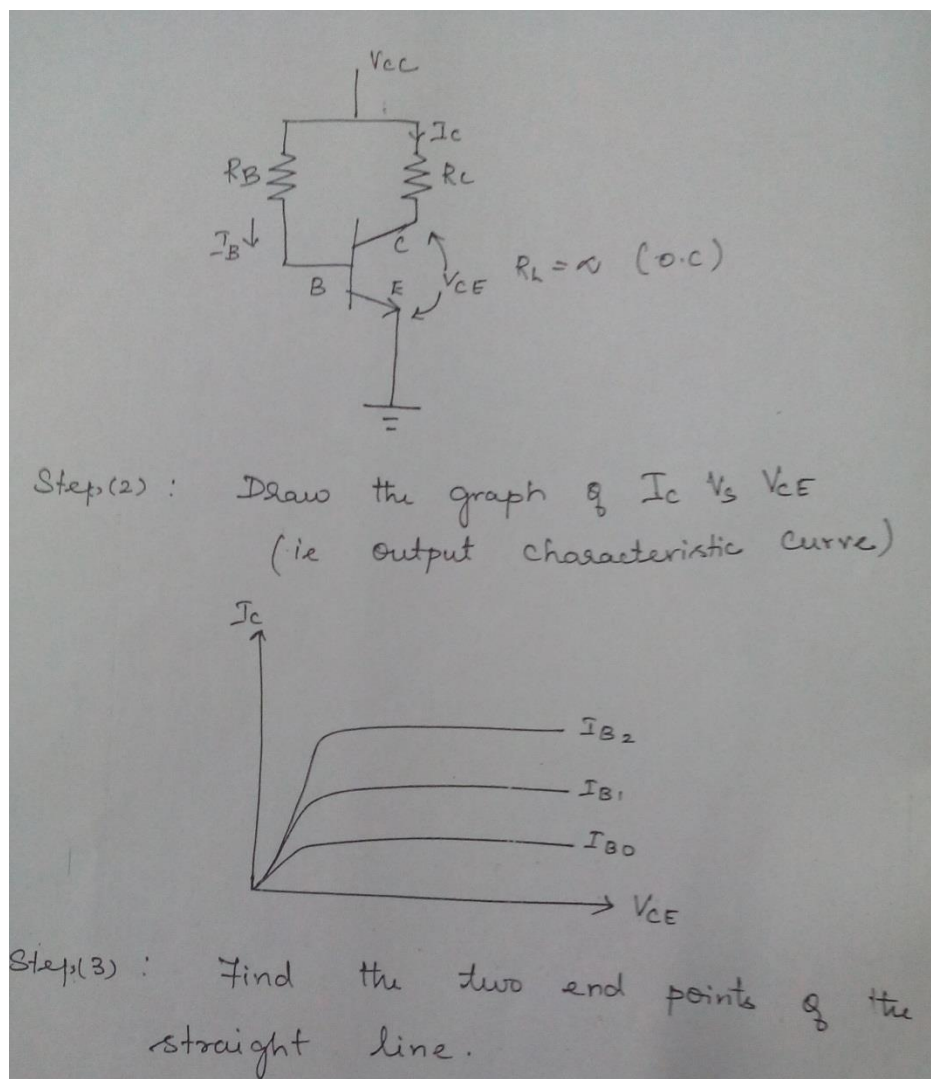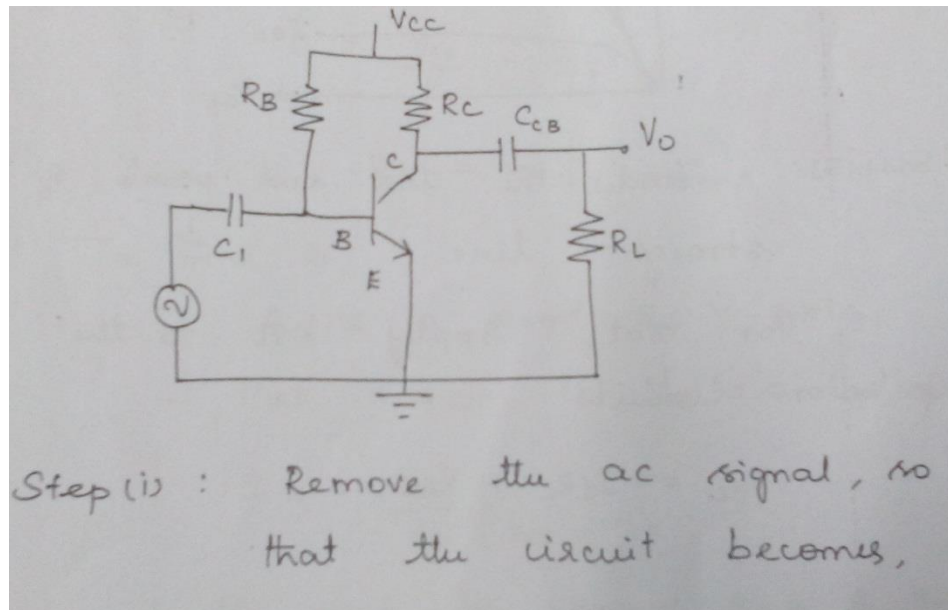Consider the common emitter amplifier circuit shown.



For that, Apply KVL to the collector circuit.

$$V_{CC} = I_C R_C + V_{CE} \longrightarrow 1$$

W.k.t the equation for straight line is

$$y = mx + c$$

Here

$$y = I_C$$

$$x = V_{CE}$$

From equation (1),

$$I_C R_C = V_{CC} - V_{CE}$$

$$I_C = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C} \longrightarrow 2$$

To find A:

A is a point on X-axis

Put $Y = 0$, ie $I_C = 0$ in equation 2

$$0 = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C}$$

$$V_{CE} = V_{CC} | I_{C=0mA}$$

To find B:

B is a point of Y – axis

Put $X = 0$, ie $V_{CE} = 0$ in equation 2

$$I_C = \frac{V_{CC}}{R_C} | V_{CE=0}$$

Finally plot the points A & B on the curve.

Step(4):

Select the I_B curve so as to find the Q – point.

To find I_B :

Apply KVL to base circuit.

$$V_{CC} = I_B R_B + V_{BE}$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

For silicon transistor $V_{BE} = 0.7V$

If V_{CC}, R_B is known, the value of I_B can be found.

Example:


$$V_{CC} = 20V, R_B = 5K, I_B = 3mA$$

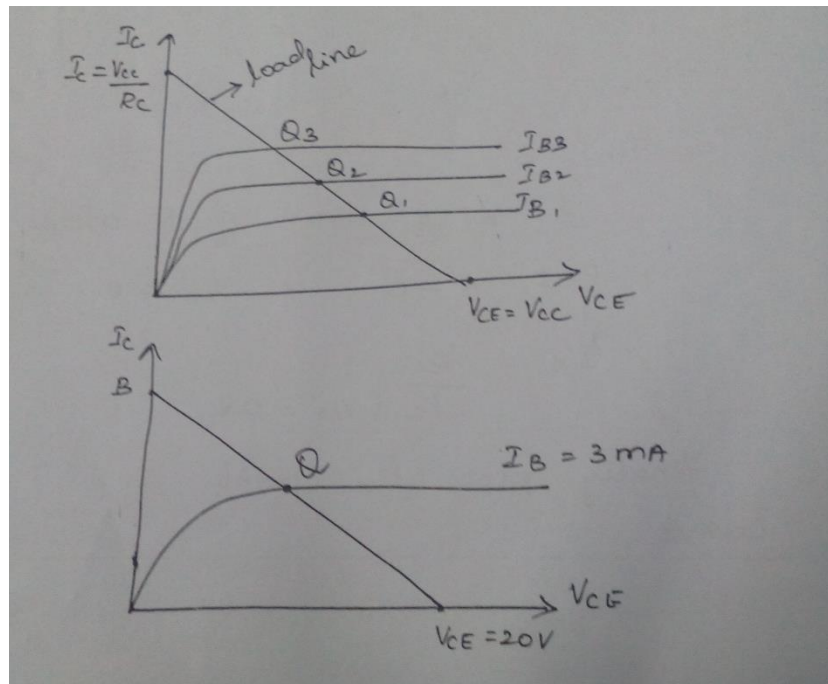

Conclusion:

Thus the intersection of DC load line and I_B curve is called as Q – Point.


Problem:

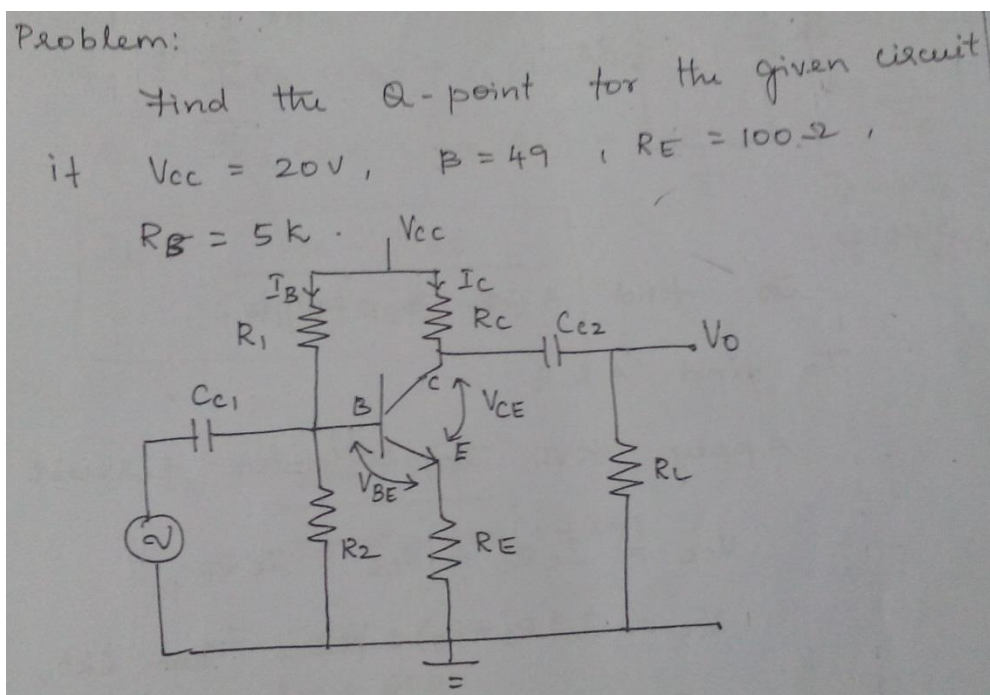

Solution:

Step(i):

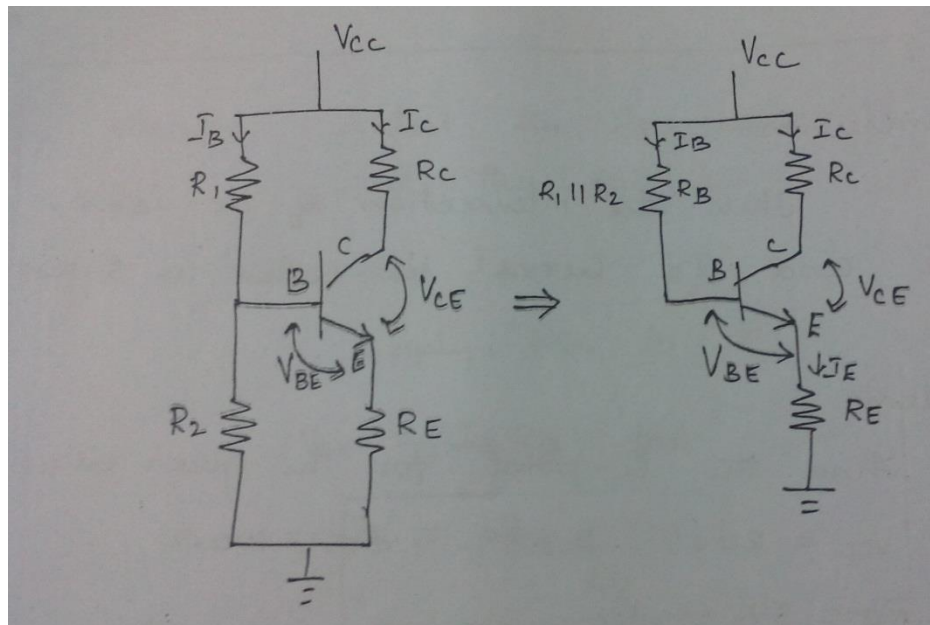Remove the AC source and redraw the circuit.



Step(2):

To find A & B points:

To find A & B:

Apply KVL to collector circuit.

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CC} = I_C (R_C + R_E) + V_{CE}$$

From CKT,

$$I_E = I_B + I_C$$

$$I_E = I_C$$

$$I_E \ll I_C$$

$$I_C = \frac{V_{CC}}{R_C + R_E} - \frac{V_{CE}}{R_C + R_E}$$

Since A is a point of X-axis,

$$I_C = 0$$

$$V_{CE} = V_{CC} | I_C=0 \text{ (Point A)}$$

Since B is a point of Y-axis,

$$V_{CE} = 0$$

$$I_C = \frac{V_{CC}}{R_C + R_E} \quad | \quad V_{CE} = 0 \quad (\text{Point B})$$

Step (3):

To find I_B curve.

Apply KVL to base circuit.

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$V_{CC} = I_B (R_B + (1 + \beta) R_E) + V_{BE}$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + R_E (1 + \beta)}$$

$$I_B = \frac{20 - V_{BE}}{5 \times 10^3 + 100(1 + 49)}$$

$$I_B = \frac{20}{5K + 5000}$$

$$I_B = 2mA$$

Step (4):

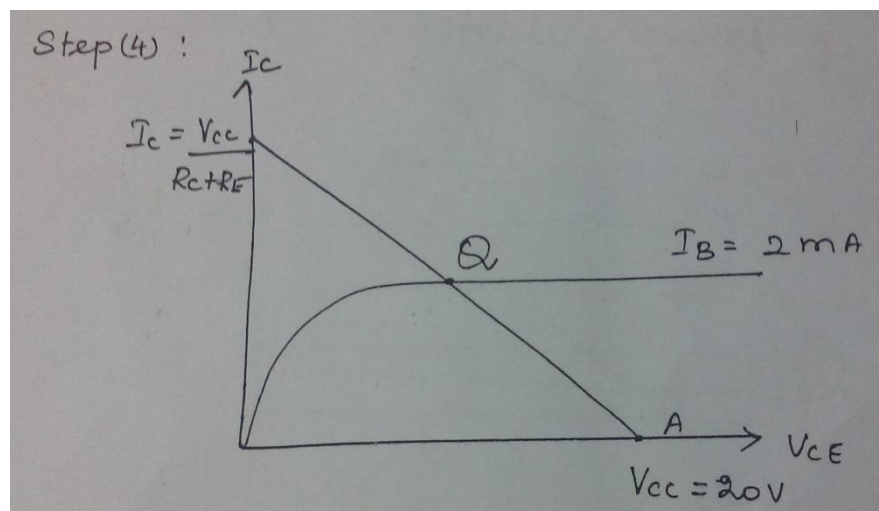

SELECTION OF OPERATING POINT FOR A.C INPUT SIGNAL:


The operating point can be selected at three different positions on the DC load line:

- Near saturation region
- Near cut-off region
- At the centre ie. Active region

Case (1):

NEAR SATURATION REGION:

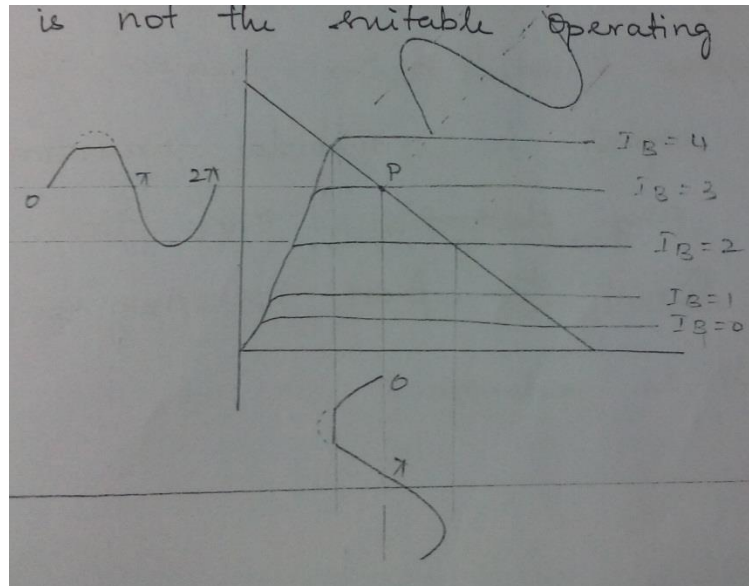
If the biasing circuit is designed to fix the Q – point (P) very near to saturation region, the collector current is clipped at the positive half cycle. Thus because of the distortions present at the collector current, point P is not the suitable operating point.



Case(ii):

NEAR CUT-OFF REGION:

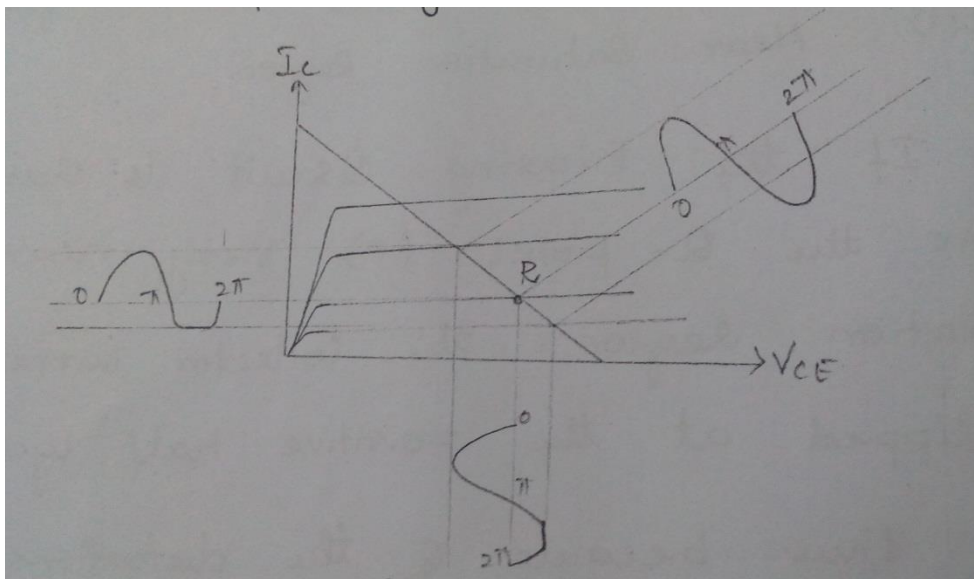
If the biasing circuit is designed to fix the Q – point (R) near cut-off region, the collector current is clipped at the negative half cycle. Thus Q-point R is also not a suitable operating point.



Case(iii):

AT ACTIVE REGION:

 If the Q – point is fixed at the centre of the active region, the output signal is sinusoidal waveform without any distortion. Thus the point Q is the best operating point.



Bias stabilization:

While designing the biasing circuit, case should be taken so that the operating point will not shift into an undesirable region (ie into cut-off or saturation region)

Factors to be considered while designing the basing circuit:

- Temperature dependent factors (I_{CO}, V_{BE})
- β or h_{fe} – Transistor current gain

I_{CO} :

The flow of current in the circuit produces heat at the junctions. This heat increases the temperature at the junctions.

Since the minority carriers are temperature dependent (I_{CO} gets doubled for every 10°C raise in temperature), they increase with the temperature. This in turn increases the I_C and hence Q – point gets shifted

V_{BE} :

- V_{BE} changes with temperature at the rate of $2.5\text{mV}/^\circ\text{C}$
- I_B depends on V_{BE}

Since $\frac{I_C}{I_B} = \beta$


$I_C = \beta I_B$, increase in I_B

Increase I_C This in turn changes the operation point.

Transistor current gain β :

The transistor parameters among different units of same type, same number changes. i.e. If we take two transistor units of same type (ie. Same number, construction, parameter specified etc.) and we them in the circuit, there is change in the β value in actual practice.

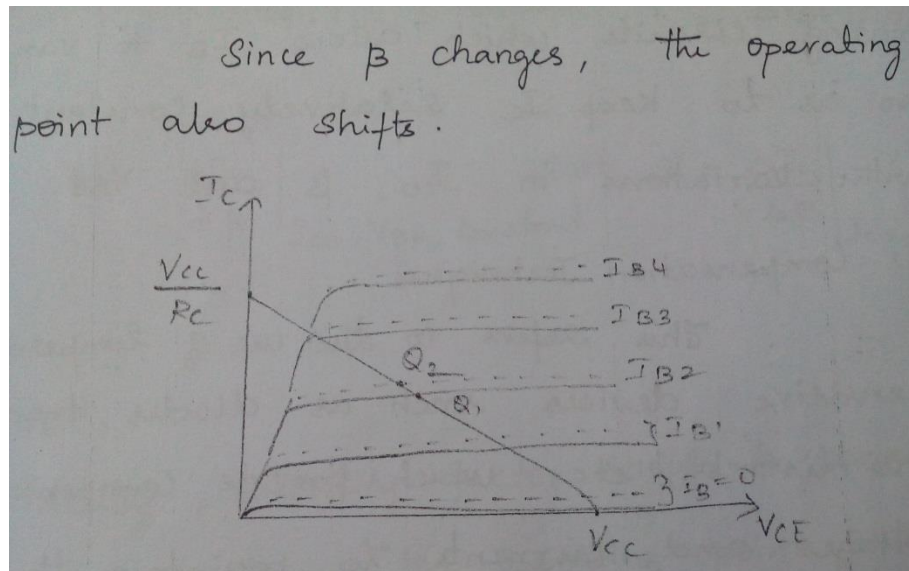The biasing circuit is designed according to the required β value. Since β changes, the operating point also shifts.



REQUIREMENTS OF A BIASING CIRCUIT:

- The emitter-base junction must be forward biased and collector-base junction must be reversed biased. i.e. The transistors should be operated in the active region.
- The circuit design should provide a degree of temperature stability.
- The operating point should be made independent of transistor parameters (like β)
- Techniques used to maintain the Q – point stable:

STABILIZATION TECHNIQUE:

This refers to the use of resistive biasing circuits which allow I_B to vary so as to keep I_C Relatively constant with variations in I_{CO} , β and V_{BE}

COMPENSATION TECHNIQUE:

This refers to the use of temperature sensitive devices such as diodes, transistors, thermistors, etc, which provide compensating voltages and current to maintain the operating point stable.

STABILITY FACTORS:

- The stability factor is a measure of stability provided by the biasing circuit.
- Stability factor indicates the degree of change in operating point due to variation in temperature.
- Since there are 3 temperature dependent variables, there are 3 stability factors.

$$S = \frac{\partial I_C}{\partial I_{CO}} \Big|_{V_{BE}, \beta \text{ constant}} \quad (\text{or}) \quad S = \frac{\Delta I_C}{\Delta I_{CO}} \Big|_{V_{BE}, \beta \text{ constant}}$$

$$S' = \frac{\partial I_C}{\partial V_{BE}} \Big|_{I_{CO}, \beta \text{ constant}} \quad (\text{or}) \quad S' = \frac{\Delta I_C}{\Delta V_{BE}} \Big|_{I_{CO}, \beta \text{ constant}}$$

$$S'' = \frac{\partial I_C}{\partial \beta} \Big|_{V_{BE}, I_{CO} \text{ constant}} \quad (\text{or}) \quad S'' = \frac{\Delta I_C}{\Delta \beta} \Big|_{V_{BE}, I_{CO} \text{ constant}}$$

Note:

- Ideally, stability factor should be perfectly zero to keep the operating point stable.
- Practically stability factor should have the value as minimum as possible.

EXPRESSION FOR STABILITY FACTOR S:

For a common emitter configuration collector current is given by

$$I_C = I_{C(\text{majority})} + I_{CEO(\text{majority})}$$

WKT

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha}$$

$$I_{CEO} = (1 + \beta) I_{CBO}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

When

I_{CBO} changes by ΔI_{CBO}

I_B changes by ΔI_B

I_C changes by ΔI_C

$$\partial I_C = \beta \partial I_B + (1 + \beta) \partial I_{CBO}$$

÷ by ∂I_C

$$1 = \beta \frac{\partial I_B}{\partial I_C} + (1 + \beta) \frac{\partial I_{CBO}}{\partial I_C}$$

$$1 - \beta \frac{\partial I_B}{\partial I_C} = (1 + \beta) \frac{\partial I_{CBO}}{\partial I_C}$$

$$\frac{\partial I_{CBO}}{\partial I_C} = \frac{(1 - \beta) \frac{\partial I_B}{\partial I_C}}{(1 + \beta)}$$

$$\text{If } S = \frac{\partial I_C}{\partial I_{CBO}}$$


$$\frac{1}{S} = \frac{(1 - \beta) \frac{\partial I_B}{\partial I_C}}{(1 + \beta)}$$

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{\partial I_B}{\partial I_C}}$$

TYPES OF BIASING CIRCUIT:

- Fixed bias circuit
- Collector to base bias circuit
- Voltage divider or self bias circuit.

FIXED BIAS CIRCUIT:

 

To find I_B :

Apply KVL to the base circuit,

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \longrightarrow 1$$

$$I_B = \frac{V_{CC}}{R_B}$$

$$V_{BE} \ll V_{CC}$$

$$V_{BE} = 0.7 \text{ for si}$$

$V_{CC} \rightarrow$ fixed, $R_B \rightarrow$ fixed and hence I_B is fixed and the circuit is called as fixed bias circuit.

To find V_{CE} :

Apply KVL to the Collector circuit,

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C \longrightarrow 2$$

To find I_C :

From equation (2),

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \longrightarrow 3$$

To find S:

WKT

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{\partial I_B}{\partial I_C}}$$

$$\frac{\partial I_B}{\partial I_C} = 0$$

$$S = \frac{(1 + \beta)}{(1 - \beta)0}$$

$$S = (1 + \beta) \longrightarrow 4$$

To find S':

$$S' = \frac{\partial I_C}{\partial V_{BE}}$$

WKT,

$$I_C = I_{C(\text{majority})} + I_{CEO(\text{majority})}$$

$$I_C = \beta I_B + I_{CBO}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

Sub I_B in above equation,

$$I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right) + (1 + \beta) I_{CBO}$$

$$I_C = \frac{\beta V_{CC}}{R_B} - \frac{\beta V_{BE}}{R_B} + (1 + \beta) I_{CBO}$$

Diff. I_C WRT to V_{BE}

$$\frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B}$$

$$S' = \frac{-\beta}{R_B} \longrightarrow 5$$

To find S'' :

$$S'' = \frac{\partial I_C}{\partial \beta}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_C = \beta I_B + I_{CBO} + \beta I_{CBO}$$

Diff I_C WRT to β

$$\frac{\partial I_C}{\partial \beta} = I_B + I_{CBO}$$

$$S'' = I_B + I_{CBO}$$

$$S'' \cong I_B$$

$$S'' = I_B = \frac{I_C}{\beta} \longrightarrow 6$$

To find relation between s and S'

$$S = (1 + \beta)$$

$$S' = \frac{-\beta}{R_B}$$

To obtain S' in terms of S

Multiply and divided by $(1 + \beta)$, S'

$$S' = \frac{-\beta}{R_B} \times \frac{(1 + \beta)}{(1 + \beta)}$$

$$S' = \frac{-\beta S}{R_B(1 + \beta)} \longrightarrow 7$$

To find relation between S and S''

We have

$$S'' = \frac{I_C}{\beta}$$

$$S' = \frac{-\beta}{R_B}$$

Multiply and divided by $(1 + \beta)$, S''

$$S'' = \frac{I_C}{\beta} \times \frac{(1 + \beta)}{(1 + \beta)}$$

$$S'' = \frac{I_C S}{\beta(1 + \beta)} \longrightarrow 8$$

ADVANTAGES OF FIXED BIAS CIRCUIT:

- Circuit is simple
- The operating point can be fixed anywhere in the active region by varying the value of R_B . Thus it provides maximum flexibility.

DISADVANTAGES:

- Thermal stability is not provided by the circuit and so the Q-point varies


$$I_C = \beta I_B + I_{CBO}$$

Since I_C Q-point varies

- Circuit depends on β

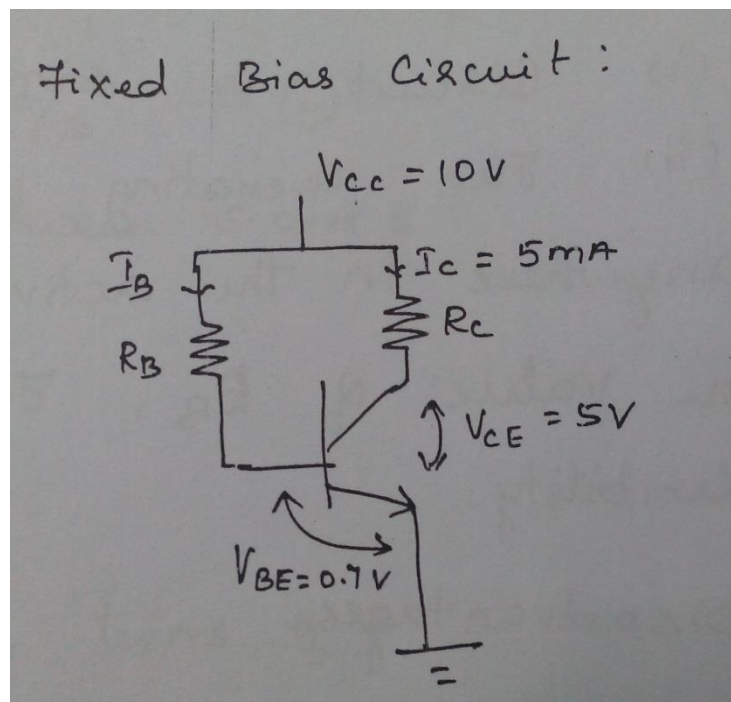Problem

Design a fixed bias circuit using a silicon transistor having β value of 100, $V_{CC} = 10V$ and DC bias conditions are to be $V_{CE} = 5V$ and $I_C = 5mA$



Solution:

Given:

$$\beta = 100$$

$$V_{CC} = 10V$$

$$V_{CE} = 5V$$

$$I_C = 5mA$$

To find:

$$R_B = ?$$

$$R_C = ?$$

$$I_B = ?$$

To find R_C :

Applying KVL to collector circuit,

$$V_{CC} = I_C R_C + V_{CE}$$

$$\frac{10}{5} = \frac{5 \times 10^{-3} R_C + 5}{5 \times 10^{-3}} = R_C$$

$$R_C = 1 \text{ K}\Omega$$

To find I_B :

$$\text{WKT } \frac{I_C}{I_B} = \beta$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{5 \text{ m}}{100}$$

$$I_B = 50 \mu\text{A}$$

To find R_B :


Applying KVL to input circuit,

$$V_{CC} = I_B R_B + V_{BE}$$


$$\frac{10 - 0.7}{50 \mu} = R_B$$

$$R_B = 1861 \text{ K}\Omega$$

Design:

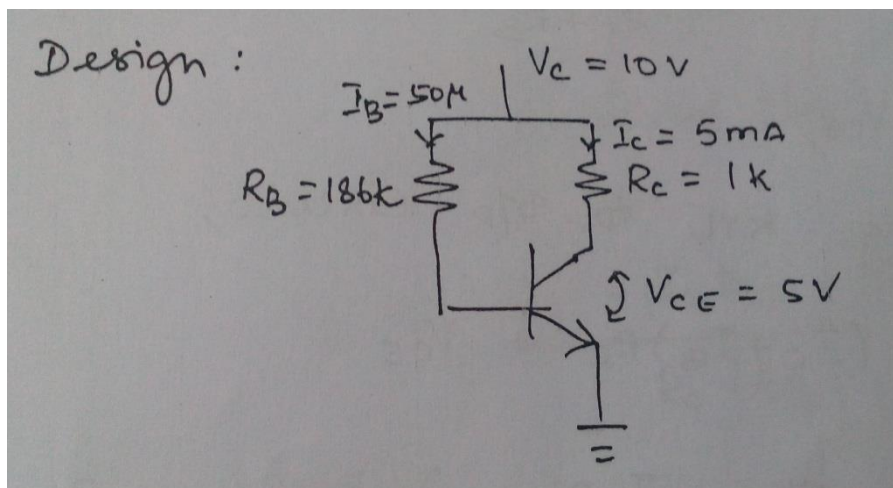

COLLECTOR TO BASE BIAS CIRCUIT:

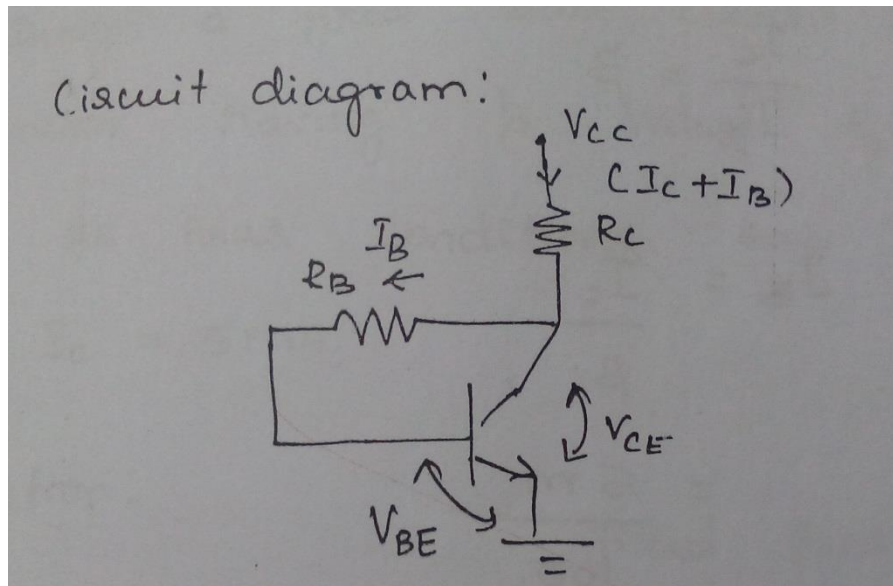

Since the R_B resistor is connected between the collector and base, it is called as collector to base bias circuit.

To find I_B :

Applying KVL to input circuit,

$$V_{CC} = (I_C + I_B)R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_C R_C + I_B (R_C + R_B) + V_{BE}$$

$$I_B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_C + R_B} \longrightarrow 1$$

To find V_{CE} :

Applying KVL to output circuit,

$$V_{CC} = (I_C + I_B)R_C + V_{CE}$$

$$V_{CC} = V_{CC} - I_C R_C - I_B R_C \longrightarrow 2$$

To find I_C :

Applying KVL to collector circuit,

$$V_{CC} = (I_C + I_B)R_C + V_{CE}$$

$$V_{CC} = I_C R_C + I_B R_C + V_{CE}$$

$$I_B = \frac{V_{CC} - V_{CE} - I_B R_C}{R_C} \longrightarrow 3$$

WKT the basic equation for I_C is

$$I_C = \beta I_B + I_{CBO}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_C \cong \beta I_B$$

To find S:

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{\partial I_B}{\partial I_C}}$$

$\frac{\partial I_B}{\partial I_C}$ is obtained by diff. I_B WRT I_C

$$I_B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_C + R_B}$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-R_C}{R_C + R_B} \longrightarrow 4$$

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{-R_C}{R_C + R_B}}$$

$$= \frac{(1 + \beta)}{(1 + \beta) \frac{R_C}{R_C + R_B}} \longrightarrow 5$$

$$S = \frac{(1 + \beta)(R_C + R_B)}{R_C + R_B + \beta R_C}$$

$$S = \frac{(1 + \beta)(R_C + R_B)}{R_B + (\beta + 1)R_C}$$

To find S':

$$S' = \frac{\partial I_C}{\partial V_{BE}}$$

$$I_B = \frac{V_{CC} - V_{CE} - I_B R_C}{R_C}$$

As there is no V_{BE} term in the above equation

WKT,

$$I_C = \beta I_B$$

Sub I_B in above equation,

$$I_C = \beta \left(\frac{V_{CC} - I_C R_C - V_{BE}}{R_C + R_B} \right)$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_C + R_B} - \frac{\beta I_C R_C}{R_C + R_B}$$

$$I_C + \frac{\beta I_C R_C}{R_C + R_B} = \frac{\beta (V_{CC} - V_{BE})}{R_C + R_B}$$

$$I_C R_B + I_C R_C + \beta I_C R_C = \beta (V_{CC} - V_{BE})$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_C + R_B + \beta R_C} \rightarrow \mathbf{5.1}$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (1 + \beta) R_C} \rightarrow \mathbf{6}$$

$$\frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B}$$

$$S' = \frac{-\beta}{R_B + (1 + \beta) R_C} \rightarrow \mathbf{7}$$

To find S'':

$$S'' = \frac{\partial I_C}{\partial \beta}$$

From equation (6),

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_C + R_B + \beta R_C}$$

$$S'' = \frac{\partial I_C}{\partial \beta}$$

$$= \frac{(R_C + R_B + \beta R_C)(V_{CC} - V_{BE}) - \beta (V_{CC} - V_{BE})(R_C)}{(R_C + R_B + \beta R_C)^2}$$

$$S'' = \frac{(V_{CC} - V_{BE})(R_C + R_B)}{(R_B + (1 + \beta) R_C)^2} \rightarrow \mathbf{8}$$

To find relation between s and S'

$$S' = \frac{-\beta}{R_B + (1 + \beta) R_C}$$

Multiply and divided by $(1 + \beta)$, $R_C + R_B$

$$S' = \frac{-\beta}{R_B + (1+\beta)R_C} \times \frac{(1+\beta)R_C + R_B}{(1+\beta)R_C + R_B} \longrightarrow 8.1$$

From equation (5),

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{-R_C}{R_C + R_B}}$$

$$= \frac{(1 + \beta)}{(1 + \beta) \frac{R_C}{R_C + R_B}}$$

$$S = \frac{(1 + \beta)(R_C + R_B)}{R_C + R_B + \beta R_C}$$

$$S = \frac{(1+\beta)(R_C+R_B)}{R_B + (\beta+1)R_C} \longrightarrow 9$$

By combining equation (9) & (8.1),

$$S' = \frac{-\beta S}{(1+\beta)R_C+R_B} \longrightarrow 10$$

To find relation between S and S''

We have

$$S'' = \frac{(V_{CC} - V_{BE})(R_C + R_B)}{(R_B + (1 + \beta)R_C)^2}$$

Multiply and divided by $(1 + \beta)$ we have

$$S'' = \frac{(V_{CC} - V_{BE})(R_C + R_B)}{(R_B + (1 + \beta)R_C)^2} \times \frac{(1 + \beta)}{(1 + \beta)}$$

$$S'' = \frac{(V_{CC} - V_{BE})S}{(1 + \beta)(R_B + (1 + \beta)R_C)}$$

$$S'' = \frac{I_C S}{\beta(1+\beta)} \longrightarrow 11$$

ADVANTAGES:


- Circuit is flexible to fix the operating point at the centre of an active region.
- Circuit is simple
- $S = 1 + \beta \rightarrow$ Fixed bias

$$S = \frac{(1+\beta)}{(1+\beta)\frac{R_C}{R_C+R_B}} \rightarrow \text{For collector to base bias}$$

Thus S is small for collector to base bias circuit, hence this provides better stability than fixed bias circuit.

Q- Point is stable:

$$I_C = \beta I_B + I_{CEO}$$

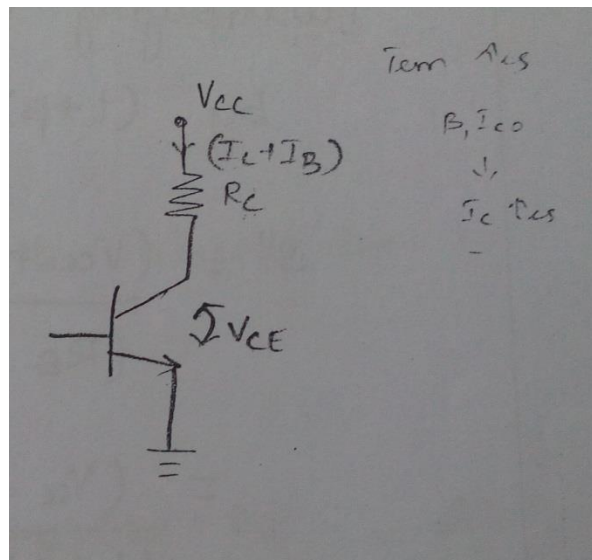

If β, I_{CEO} increases

I_C increases

Drop across R_C increases


V_{CE} decrease [$V_{CC} = V_{CC} - I_C R_C + I_B R_C$]

I_B decrease [$I_B = \frac{V_{CC} - V_{CE} - I_C R_C}{R_B}$]

I_C decrease [$I_C = \beta I_B$]


Thus the original increase is compensated and Q - Point remains stable.

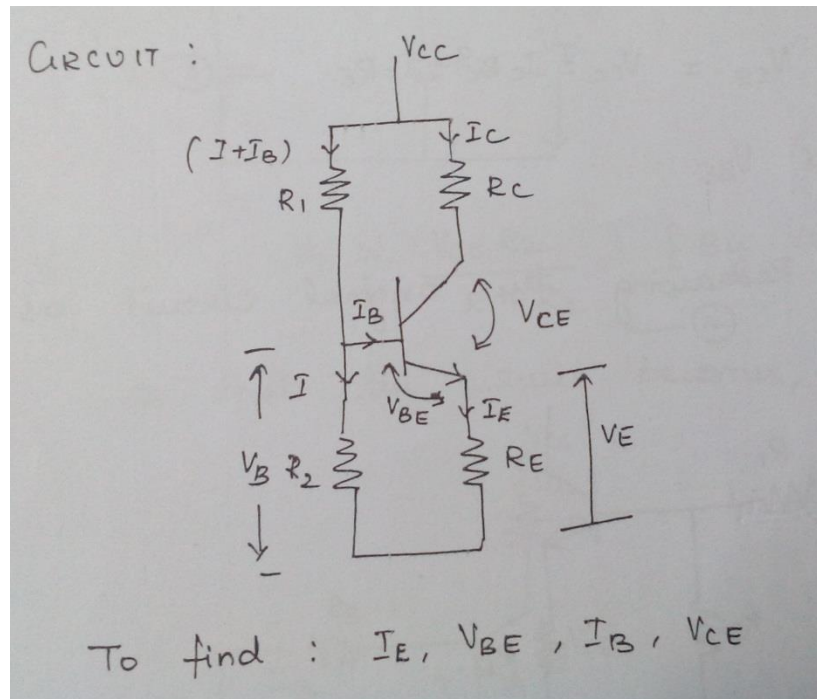**VOLTAGE-DIVIDER BIAS CIRCUIT:
[OR]
SELF - BIAS (OR) EMITTER BIAS CIRCUIT.**



To find I_E :

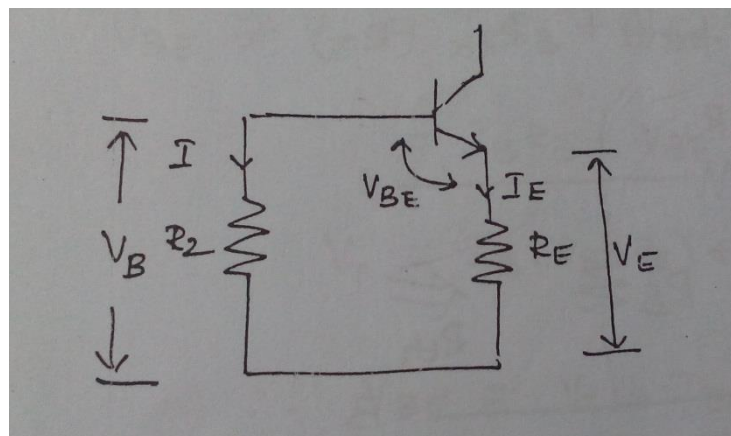Consider the closed loop shown in the circuit.



$$V_B = V_{BE} + V_E$$

$$V_B = V_{BE} + I_E R_E$$

$$I_E = \frac{V_B - V_{BE}}{R_E} \longrightarrow 1$$

To find V_{CE} :


Applying KVL to the collector circuit.

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \rightarrow 2$$


To find V_{BE} :

 Redrawing the original circuit as follow,




To find thevenin's equivalent circuit:-

To find $R_{th}(R_b)$:

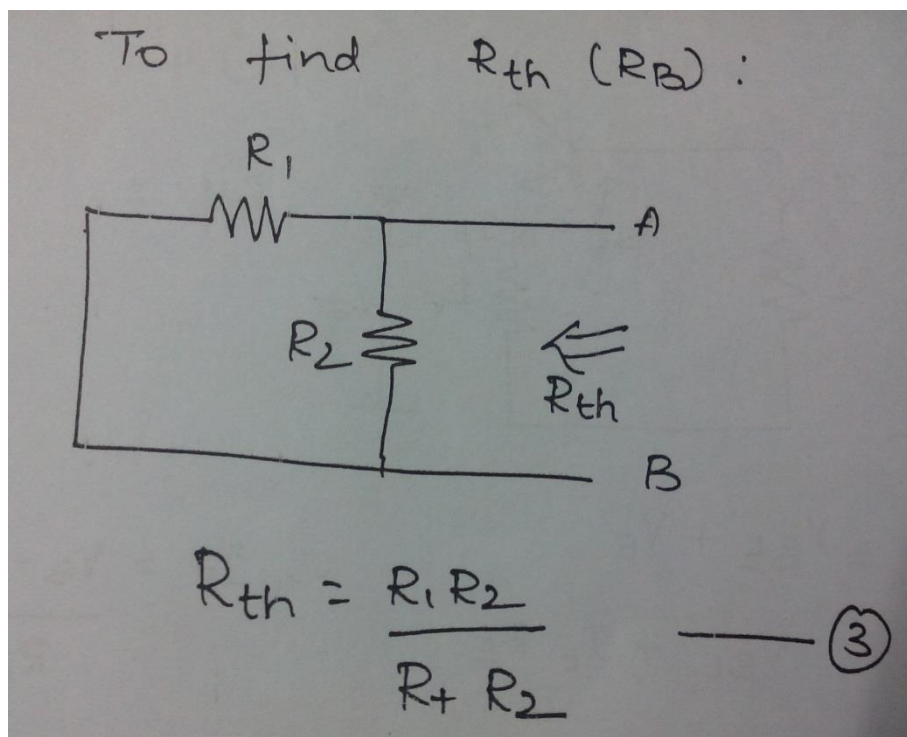


To find $V_T (V_{th})$:

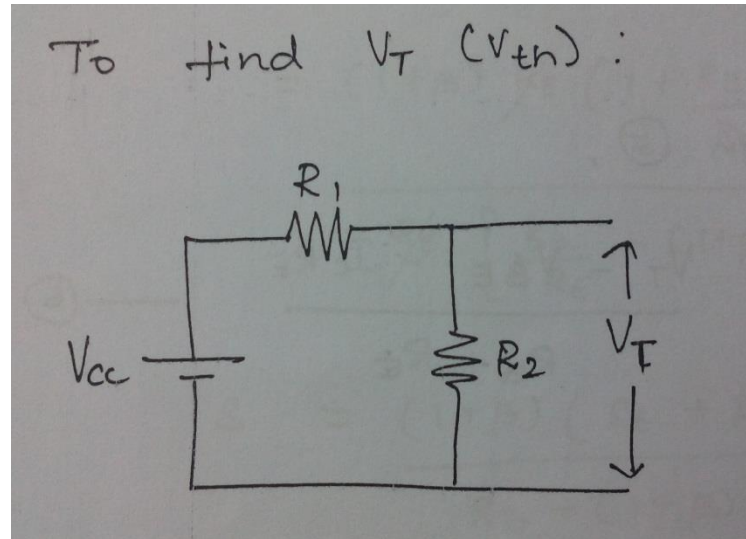

$$V_T = \frac{V_{CC}R_2}{R_1+R_2} \rightarrow 4$$

By voltage divided rule.

So that the circuit becomes,

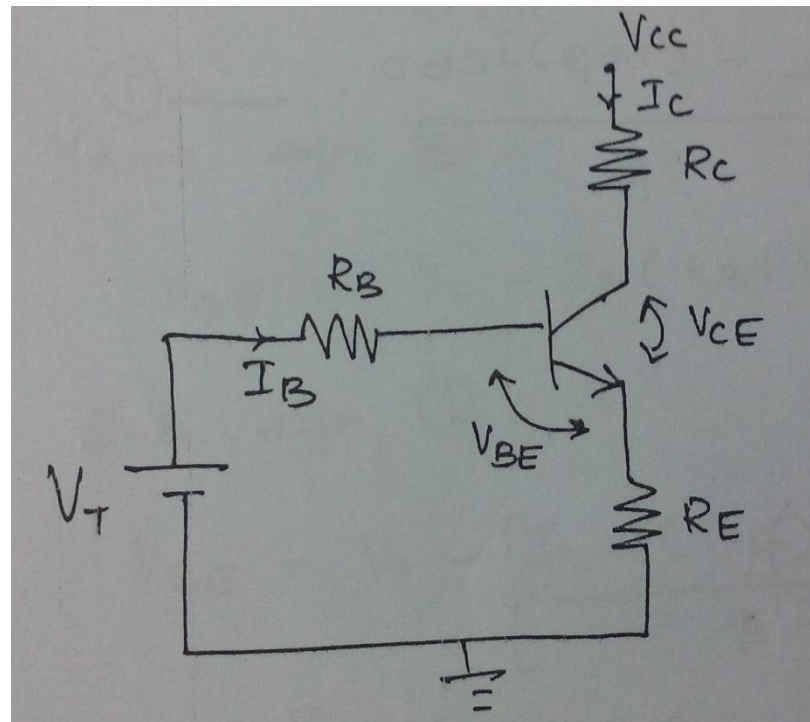

Thus,

$$V_{BC} \rightarrow V_T = I_B R_B + V_{BE} + I_E R_E$$

$$= I_B R_B + V_{BE} + (I_B + I_C) R_E$$

$$I_E = I_B + I_C$$

$$V_T = I_B(R_B + R_E) + V_{BE} + I_C R_E$$

$$V_{BE} = V_T - I_B(R_B + R_E) + I_C R_E \longrightarrow 5$$

To find I_B :

From equation (5)

$$I_B = \frac{V_T - V_{BE} - I_C R_E}{R_B + R_E} \longrightarrow 6$$

To find S :

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_B = \frac{I_C - (1 + \beta) I_{CBO}}{\beta} \longrightarrow 7$$

WKT

$$\frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_B + R_E}$$

$$S = \frac{(1 + \beta)}{(1 - \beta) \frac{-R_E}{R_B + R_E}}$$

$$= \frac{(1 + \beta)}{(1 - \beta) \frac{-R_E}{R_B + R_E}}$$

$$S = \frac{(1 + \beta)(R_B + R_E)}{R_B + R_E + \beta R_E}$$

$$S = \frac{(1 + \beta)(R_B + R_E)}{R_B + (\beta + 1)R_E} \longrightarrow 8$$

To find S' :

$$\frac{\partial I_C}{\partial V_{BE}}$$

From equation (7),

$$V_{BE} = V_T + I_B(R_B + R_E) - I_C R_E$$

Sub equation (7),

$$V_{BE} = V_T + \frac{I_C - (1 + \beta) I_{CBO}}{\beta} (R_B + R_E) - I_C R_E$$

$$V_{BE} = V_T + \frac{I_C}{\beta}(R_B + R_E) + \frac{(1 + \beta) I_{CBO}}{\beta}(R_B + R_E) - I_C R_E$$

$$V_{BE} = V_T + \frac{I_C}{\beta}(R_B + R_E) + \frac{(1 + \beta) I_{CBO}(R_B + R_E)}{\beta} - \frac{I_C R_E \beta}{\beta}$$

$$V_{BE} = V_T + \frac{I_C(R_B + R_E(1 + \beta))}{\beta} + \frac{(1 + \beta) I_{CBO}(R_B + R_E)}{\beta}$$

Let

$$V' = \frac{(1 + \beta) I_{CBO}(R_B + R_E)}{\beta}$$

$$V_{BE} = V_T + \frac{I_C(R_B + R_E(1 + \beta))}{\beta} + V'$$

$$\frac{I_C(R_B + R_E(1 + \beta))}{\beta} = V_T - V_{BE} + V'$$

$$I_C = \frac{\beta[V_T - V_{BE} + V']}{R_B + (\beta + 1)R_E} \longrightarrow 9$$

$$sS' = \frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B + (\beta + 1)R_E} \longrightarrow 10$$

To find S'' :

$$S'' = \frac{\partial I_C}{\partial \beta}$$

Differentiating equation (9), WRT β

$$S'' = \frac{R_B + R_E(1 + \beta)[V_T - V_{BE} + V'] - \beta[V_T - V_{BE} + V']R_E}{[R_B + R_E(1 + \beta)]^2}$$

$$S'' = \frac{(R_B + R_E)[V_T - V_{BE} + V']}{[R_B + R_E(1 + \beta)]^2}$$

Now multiply and divide by $(1 + \beta)$

$$S'' = \frac{(R_B + R_E)[V_T - V_{BE} + V']}{[R_B + R_E(1 + \beta)]^2} \times \frac{(1 + \beta)}{(1 + \beta)}$$

$$S'' = \frac{S[V_T - V_{BE} + V']}{(1 + \beta)R_B + R_E(1 + \beta)}$$

$$S'' = \frac{I_C S}{\beta(1 + \beta)} \text{ by equation (9)} \longrightarrow 11$$

Relation between S and S'

$$S = \frac{(1 + \beta)(R_B + R_E)}{R_B + (\beta + 1)R_E}$$

$$S' = \frac{-\beta}{R_B + (\beta + 1)R_E}$$

Multiply and divide by $(1 + \beta)(R_B + R_E)$

$$S' = \frac{-\beta}{R_B + (\beta + 1)R_E} \times \frac{(1 + \beta)(R_B + R_E)}{(1 + \beta)(R_B + R_E)}$$

$$S' = \frac{-\beta S}{(1 + \beta)(R_B + R_E)} \longrightarrow 12$$

Relation between S and S''


$$S'' = \frac{I_C S}{\beta(1 + \beta)} \text{ by equation (11)}$$

BIAS COMPENSATION:

Compensation techniques use temperature sensitive devices such as diode, transistors, thermistors, sensistors etc. to maintain operating point constant.

THERMISTOR COMPENSATION:

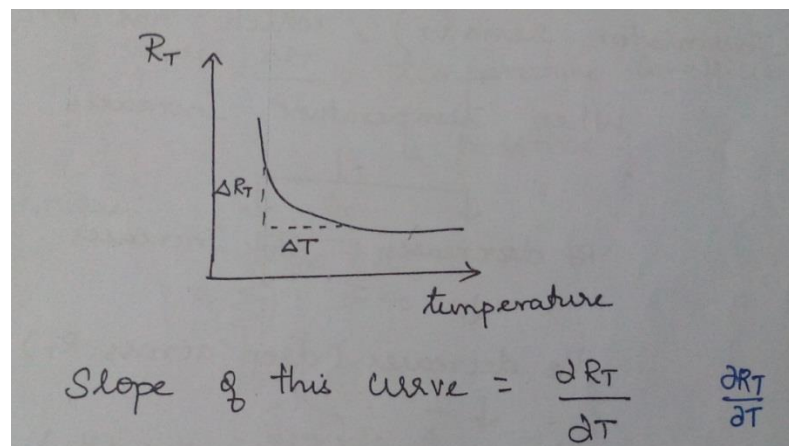Thermistors have a negative temperature co-efficient ie. Its resistance decrease exponentially with increase in temperature as shown below.



Slope of this curve = $\frac{\partial R_T}{\partial T}$

Where $\frac{\partial R_T}{\partial T} \rightarrow$ temperature coefficient for thermistor.


It is negative.

Therefore, thermistors are said to have negative temperature coefficient of resistance (NTC).


FIRST TYPE:

COMPENSATION TECHNIQUE:

Consider the circuit shown below.

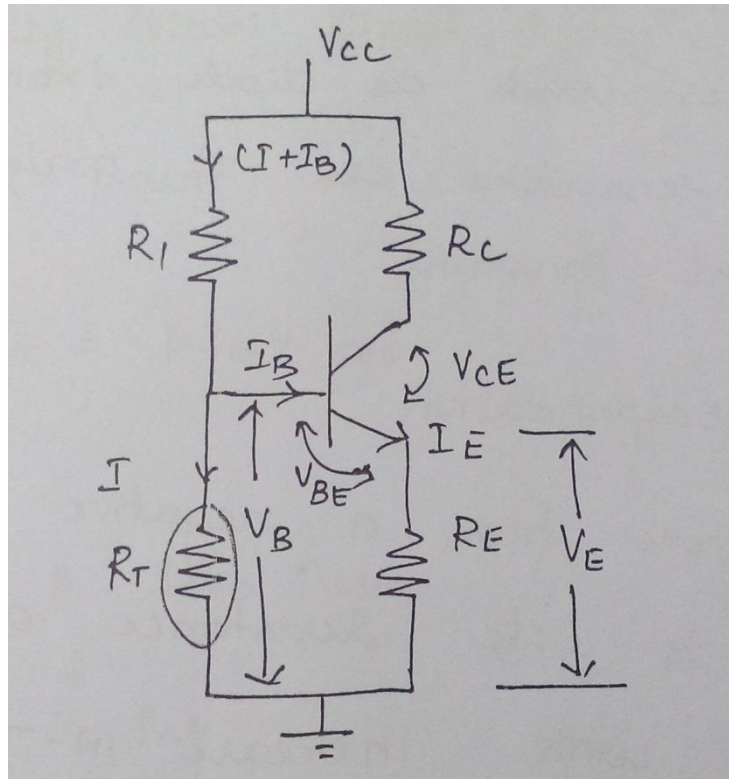

 
Here in the circuit, R_T is R_b (Thermistor resistor), which has NTC.




$$I_C = \beta I_B$$

Thus the original increase in I_C is compensated and Q- Point is made stable.

SECOND TYPE:

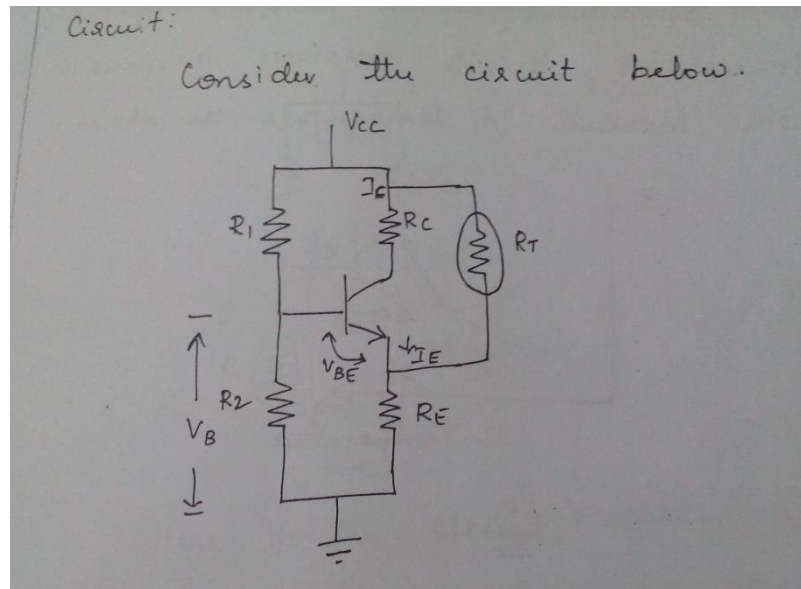


Explanation:

 

Thus the original increase in I_C is compensated and Q- Point is maintain.



Sensistor compensation technique:

 Sensistors have a positive temperature co-efficient ie. Its resistance increase with increase in temperature as shown.





Where $\frac{\Delta R_T}{\Delta T}$ = temperature co-efficient

= is positive

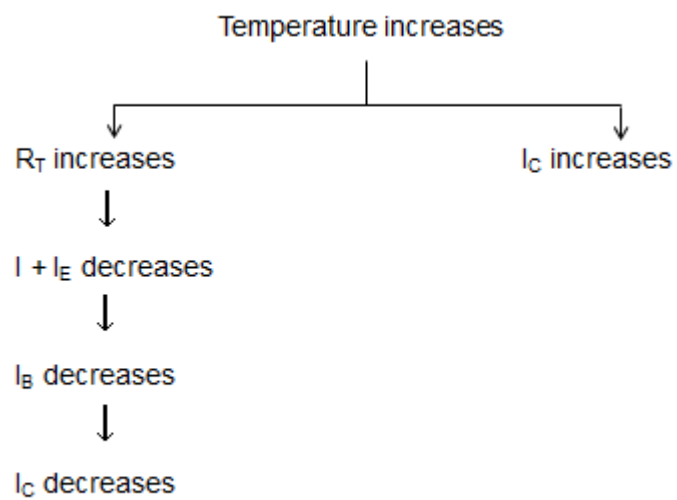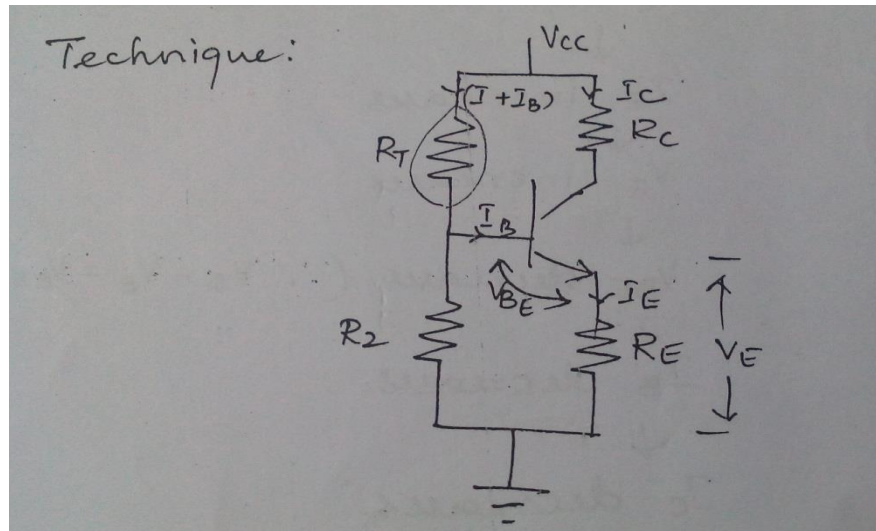

Thus the variation in I_C is compensated.

DIODE COMPENSATION FOR V_{BE} :

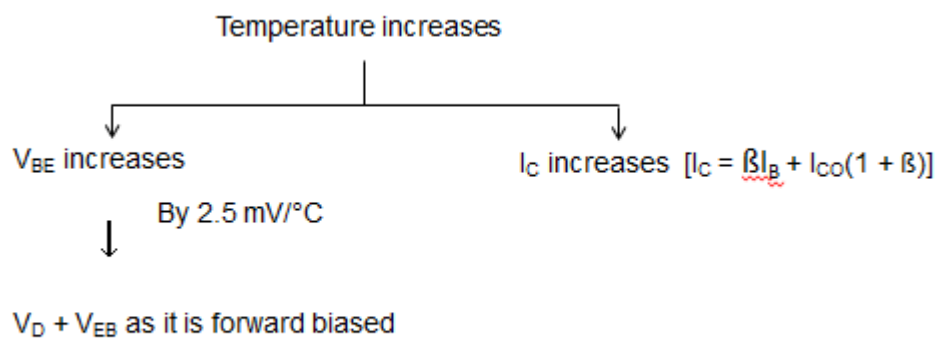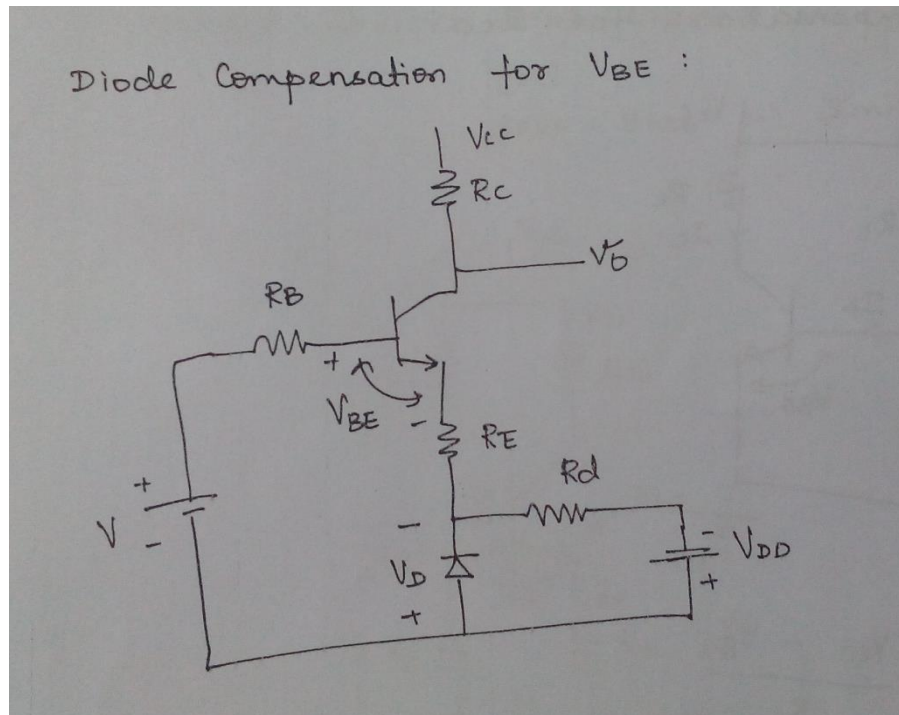


Thus the variation in V_{BE} is cancelled due to V_D (Reverse polarity)

$$V_{BE} = V + I_B R_B + V_E + V_D$$

$$V = I_B R_B + V_E - V_D$$

DIODE COMPENSATION FOR I_{CO} :

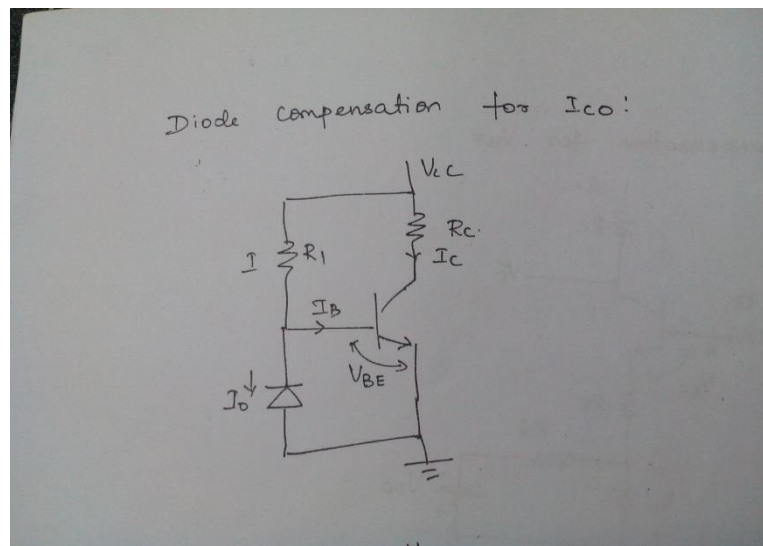

$$I = \frac{V_{CC} - V_{BE}}{R_1}$$

$$I = \frac{V_{CC}}{R_1} [V_{BE} \cong 0.2 \text{ for Ge}]$$

$$I_B = I + I_o$$

WKT,

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_C = \beta(I - I_o) + (1 + \beta) I_{CBO}$$

$$I_C = \beta I - \beta I_o + \beta I_{CBO} + I_{CBO}$$

FET BIASING:

The general relationship that can be applied to the DC analysis of all FET amplifiers are

$$I_q \cong 0A$$

$$I_D = I_S$$

For JFETS and depletion -type MOSFETS shockley's equation is applied to relate the input and output quantities:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

For enhancement - type MOSFET'S the following equation is applied:

$$I_D = K((V_{GS} - V_T)^2)$$

Where

I_{DD} – Reverse saturation current

V_P – Pinch of voltage

FIXED BIAS CONFIGURATION

Consider the configuration shown below which includes the AC levels v_i and V_o and the coupling capacitors (C_1 and C_2).

For DC analysis, capacitors acts like open circuit ie. At DC , $f = 0$, capacitance = $\frac{1}{j\omega C} = \alpha$

For AC analysis, capacitors acts like short circuits.


The resistors R_G is to ensure that V_i appears at the input to the FET amplifier for AC analysis.


For dc analysis,

$$I_G \cong 0A$$

$$V_{RG} = I_G R_G = 0$$

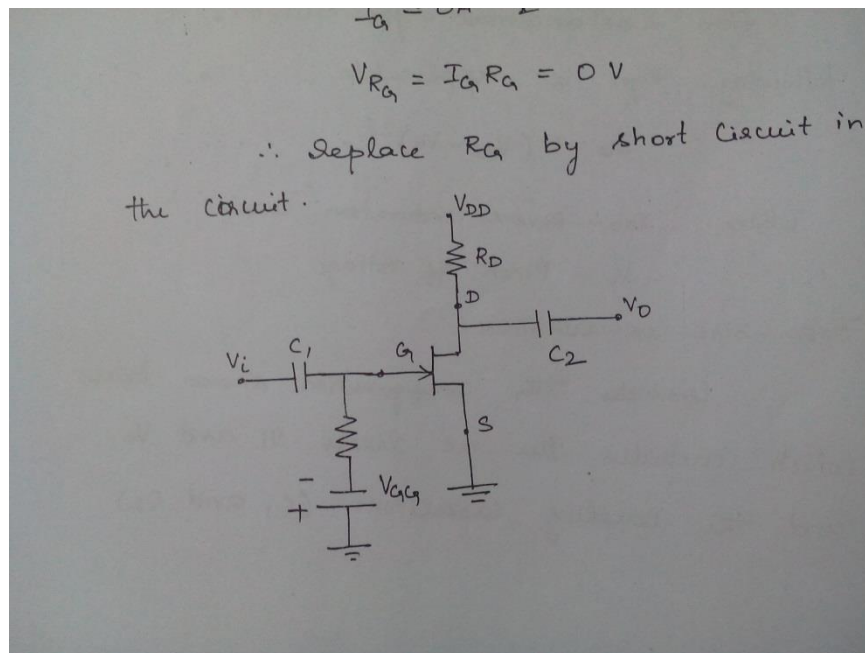Replace R_G by short circuit in the circuit.



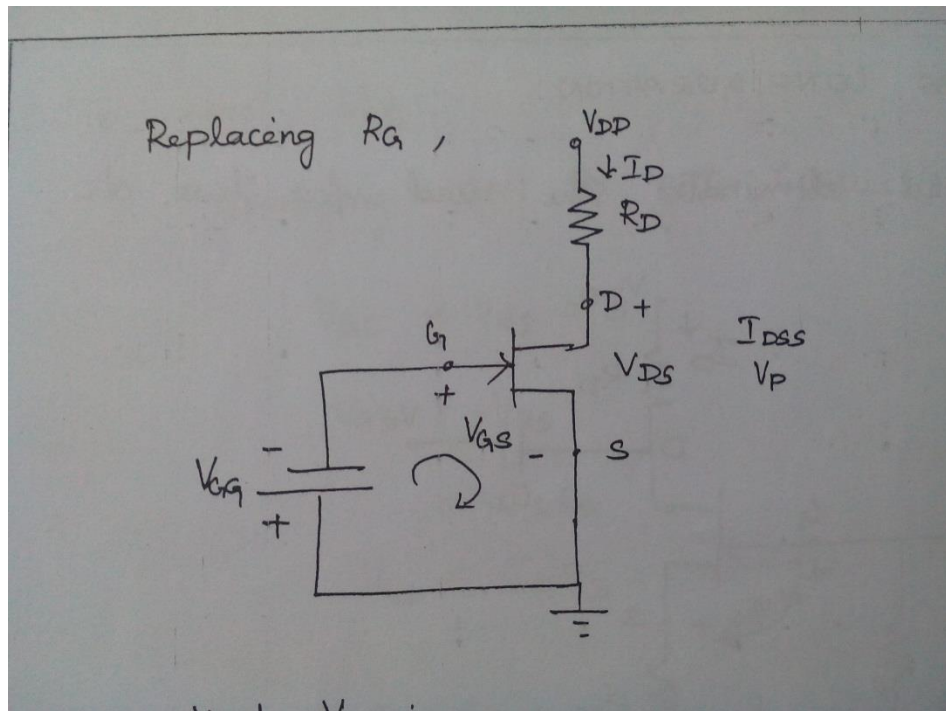

To find V_{GS}

Apply KVL to gate circuit,

$$-V_{GG} = V_{GS}$$

$$V_{GS} = -V_{GG} \rightarrow 1$$

Since V_{GG} is fixed DC supply the voltage V_{GS} is fixed in magnitude, resulting in the notation "fixed bias configuration".


To find I_D :

I_D is controlled by shockley's equation,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

SELF BIAS CONFIGURATION

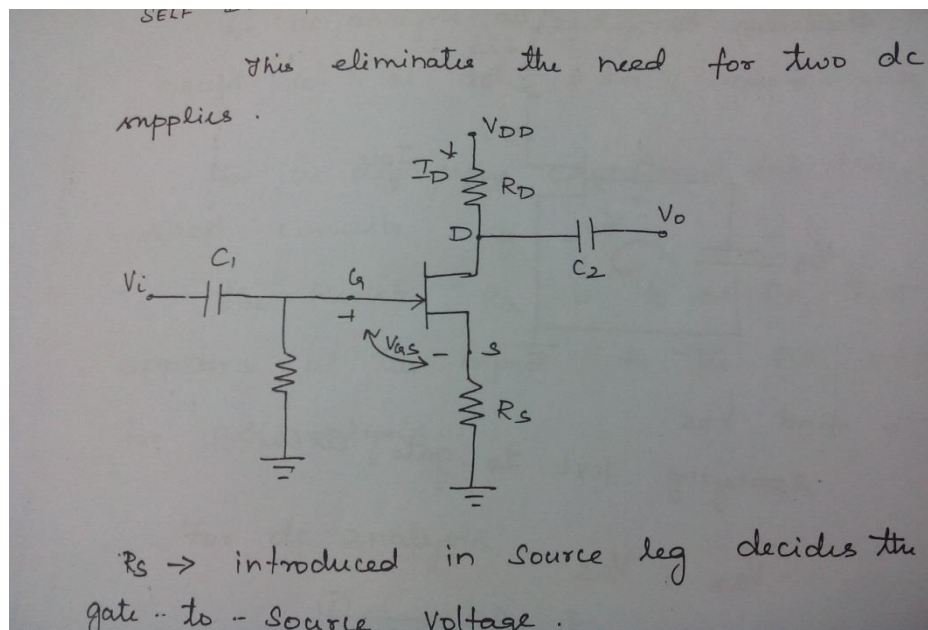
This eliminates the need for two DC suppliers.



DC analysis:

For DC analysis, capacitors are replaced by 'open circuits' and the resistors R_G replaced by short-circuit since $I_G = 0A$.

Therefore the circuit reduce to,

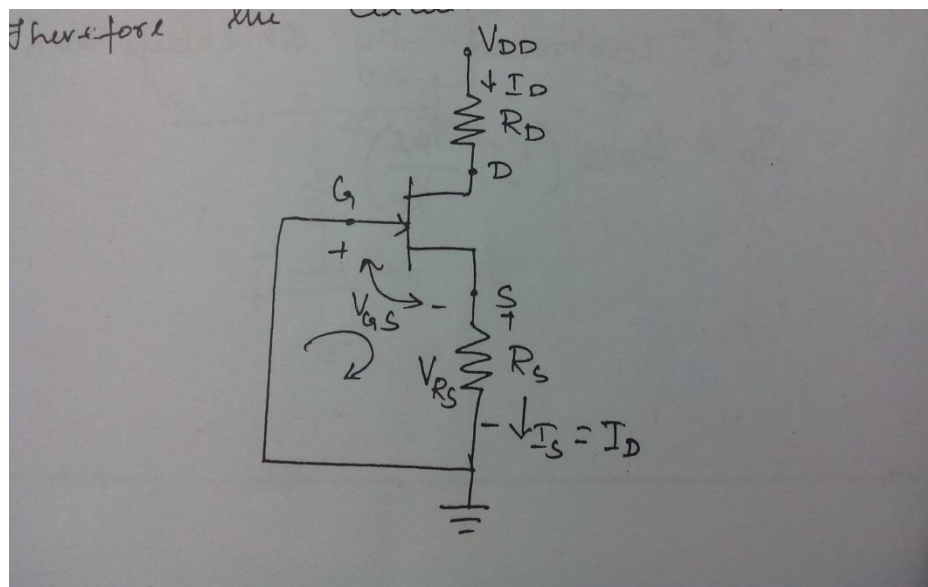

To find V_{GS} :

apply KVL to gate circuit,

$$V_{GS} + V_{RS} = 0$$

$$V_{GS} = -V_{RS}$$

$$= I_S R_S$$

$$V_{GS} = -I_D R_S \rightarrow 1$$

$V_{GS} \rightarrow$ Function of I_D and not fixed as in fixed bias.

To find I_D :

by shockley's equation,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{-I_D R_S}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2 \rightarrow 2$$

To find V_{DS} :

Apply KVL to output circuit,

$$V_{DD} = I_D R_D - V_{DS} + I_S R_S$$

$$I_S = I_D$$


$$V_{DD} = I_D R_D - V_{DS} + I_D R_S$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \rightarrow 3$$

VOLTAGE - DIVIDER BIASING:


Consider the circuit shown.

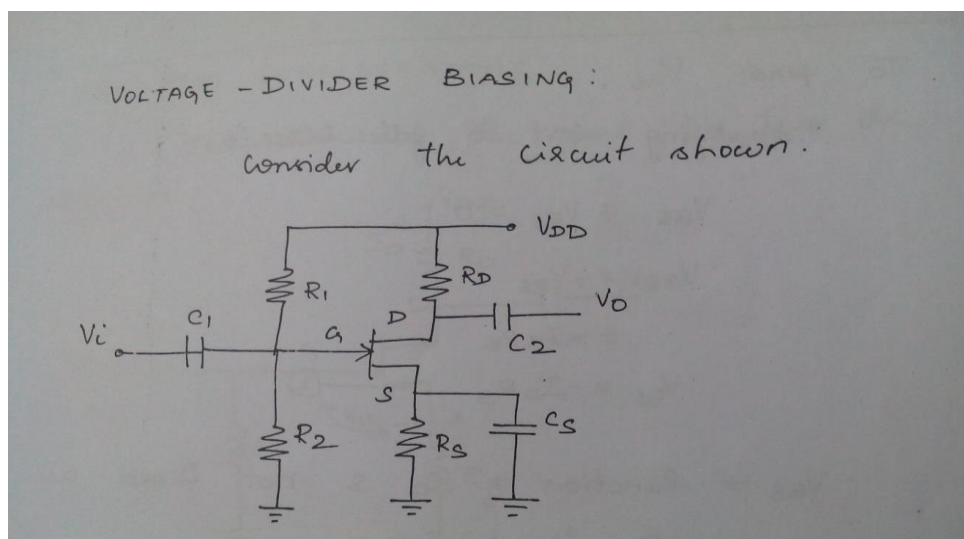

DC analysis:

- Remove the AC source
- O.C all the capacitors.

So that the circuit reduce to

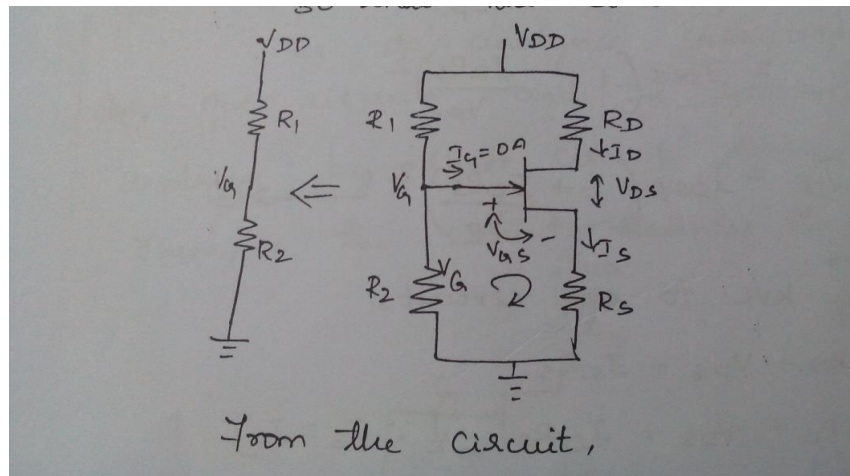

From the circuit,

$$V_G = \frac{V_{DD}R_2}{R_1+R_2} \longrightarrow 1$$

By voltage divider sub

To find V_{GS} :

apply KVL to gate circuit,

$$V_G = V_{GS} + V_{RS}$$

$$V_G = V_{GS} + I_S R_S$$

$$V_G = V_{GS} + I_D R_S$$

$$I_S = I_D$$

$$V_{GS} = V_G - I_D R_S \longrightarrow 2$$

To find V_{DS} :

Apply KVL to drain circuit,

$$V_{DD} = I_D R_D - V_{DS} + I_S R_S$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

$$I_D = I_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \longrightarrow 3$$